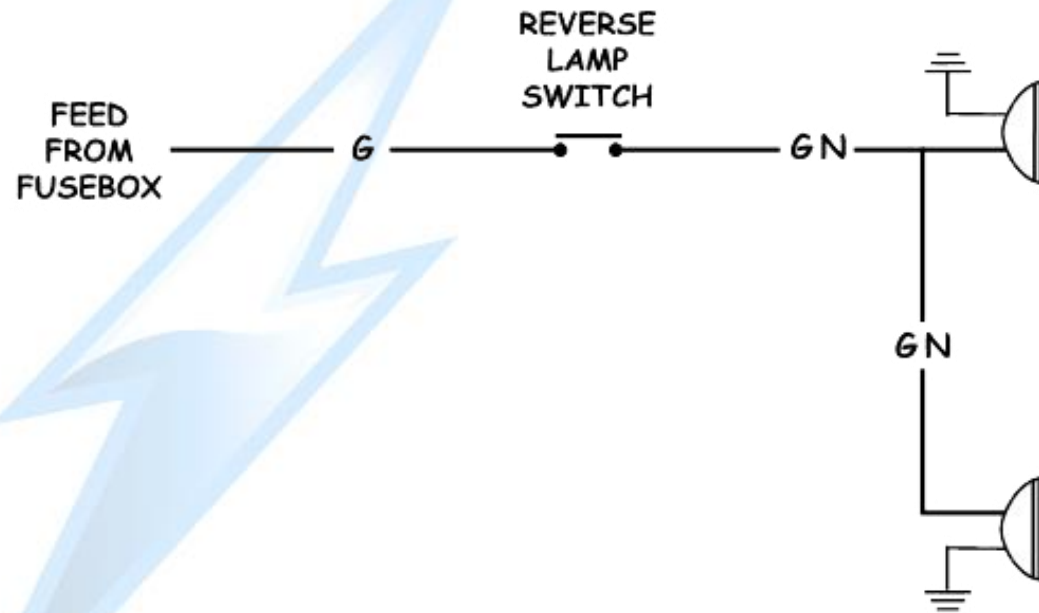


Two reverse lamps are shown. If only using one then obviously disregard the link to the second. If you are using a dash mounted switch then you should also have a warning lamp. If it is not built into the switch take a GN wire from the same position as the GN to the reverse lamp to a warning lamp and earth the bulbholder.

Do not be concerned where the G feed actually comes from. Ultimately it comes from the fused 'ignition on' side of the fusebox, but for convenience it can be linked into the G circuit at any point.

Ensure you have a good earth when fitting reverse lamps.



Standard Cable Colour Abbreviations Used as follows:

B = Black	N = Brown	R = Red	W = White
G = Green	O = Orange	S = Slate	Y = Yellow
K = Pink	P = Purple	U = Blue	LG = Lt Green

WIRING FOR REVERSE LIGHTS

